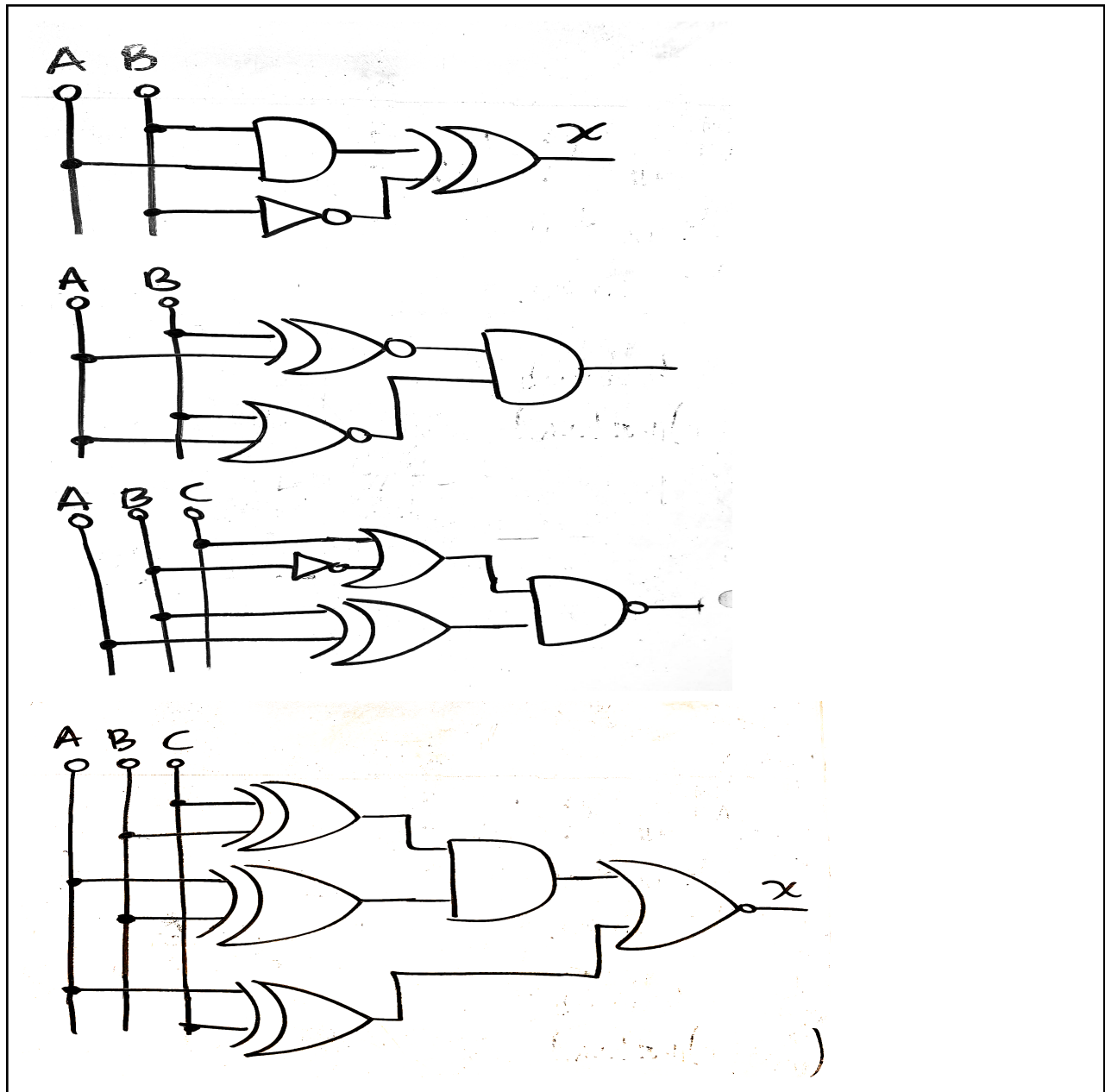



① Write the logic equation for the diagrams below:



1. $Out = (AB)XOR(notB)$
2. $Out = (not(AXORB))AND(ANORB)$
3. $Out = ((notB)ORC)NAND(AXORB)$
4. $Out = (AXORC)NOR((AXORB)AND(CXORB))$

② Draw the diagram for the logic equations below:

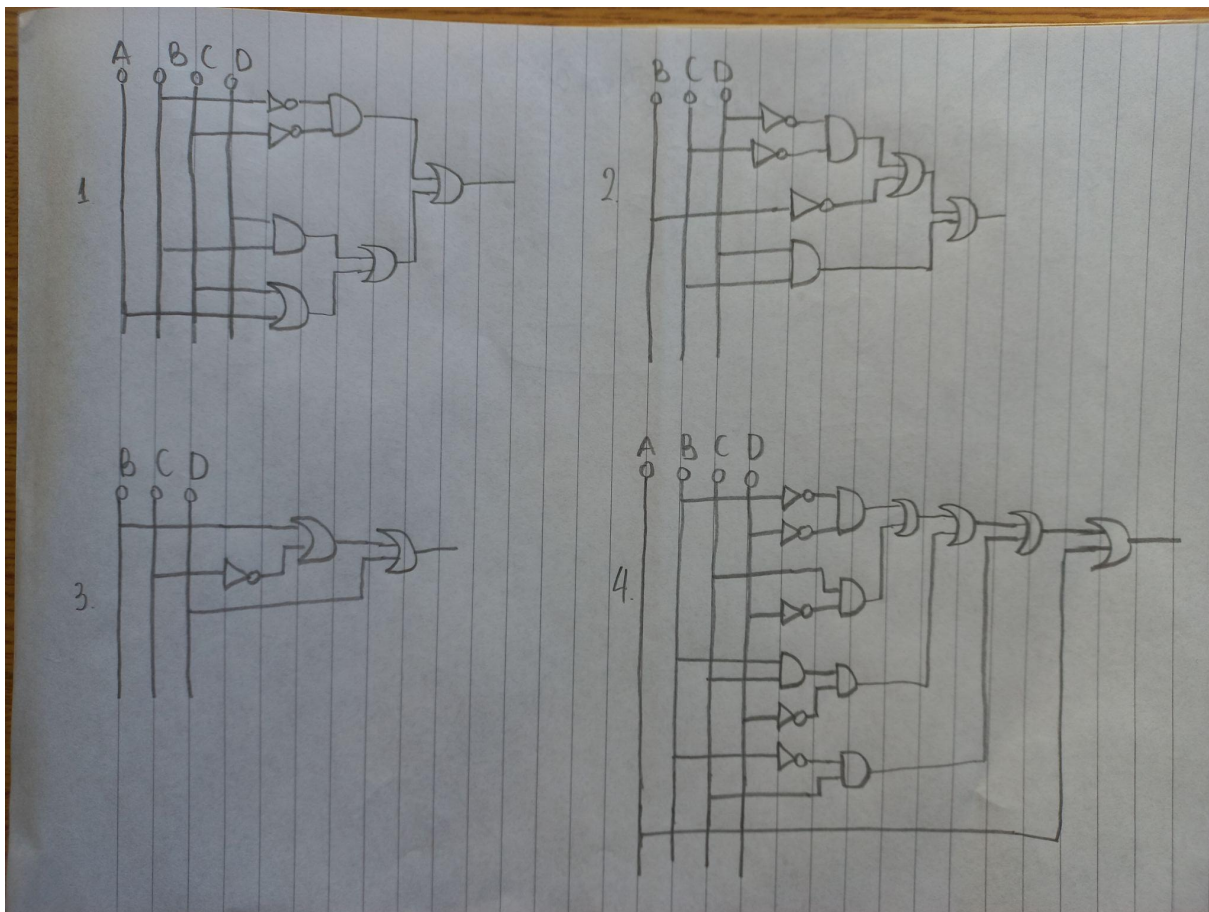1. $Out1 = A + C + BD + (notB notD)$
2. $Out2 = notB + (notC notD) + CD$
3. $Out3 = B + notC + D$
4. $Out4 = (notB notD) + (C notD) + (BCnotD) + (notB C) + A$



③ Simplify the K-map Tables below and write the logical equations:

Table 1

ab/ c	00	01	11	10
0		1		
1		1	1	

Out = $\text{not}AB + CB$

Table 2

ab/ c	00	01	11	10
0		1		1
1		1	1	1

Out = $\text{not}AB + \text{Anot}B + CB + CA$

Table 3

ab/ c	00	01	11	10
0	1			1
1	1			1

$$\text{Out} = \text{notAnotB} + \text{AnotB} + \text{notCnotB} + \text{CnotB}$$

Table 4

ab/ c	00	01	11	10
0	1	1	1	1
1			1	

$$\text{Out} = \text{notC} + \text{AB}$$

Table 1

ab/ cd	00	01	11	10
00	1			1
01				
11				
10	1			1

$$\text{Out} = \text{notCnotDnotB} + \text{CnotDnotB} + \text{notAnotBnotD} + \text{AnotBnotD}$$

- ④ The apartment below needs a notification system that sends an SMS to the owner when:
- Any of the two windows (**W1 or W2**) is open (**True = 1**) when the main door (**F**) is locked (**False = 0**), $((W1 + W2)\text{ANDnot}F)$
 - The (**B**) is open (**True = 1**) when the main (**F**) door is locked (**False = 0**), $(B\text{not}F)$
 - The TV (**T**) screen is **ON (True = 1)** when the washing machine (**M**) and the dish washing (**D**) machine are ON. $(T(MD))$

Add 2 more rules and find the equation for the notification system.

- The baranda's door (**B**) is closed and the left window is open (**W1**) $(\text{not}BW1)$
- When the kitchen (**K**), the washing machine (**M**) and the dish washing (**D**) machine are ON. (KMD)

$$\text{Out} = ((W1 + W2)\text{ANDnot}F) + (B\text{not}F) + (T(MD)) + (\text{not}BW1) + (KMD)$$

